

VIETNAM NATIONAL UNIVERSITY HO CHI  
MINH CITY HO CHI MINH CITY UNIVERSITY  
OF TECHNOLOGY FACULTY OF COMPUTER  
SCIENCE AND ENGINEERING



## **LOGIC DESIGN WITH HDL**

---

# **REPORT LAB 1**

---

Students:	Phạm Anh Tài	2350023
	Phạm Ngọc Huy	2352404
	Lục Tấn Phúc	2352935
	Trần Đình Duy Khương	2352638

HO CHI MINH CITY, 20 March 2024

## I. Exercise

### 1) Exercise 1:

a)




 


Figure 1: 1-to-2 Decoder

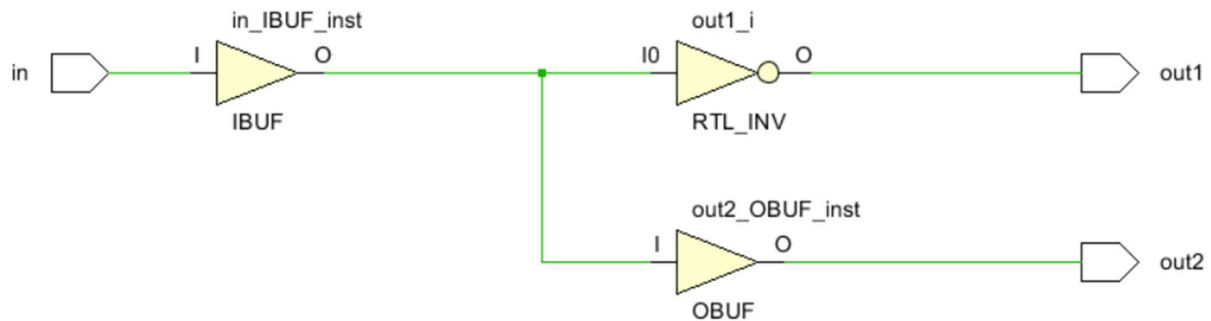

b) Design a 2-to-1 Multiplexer

 

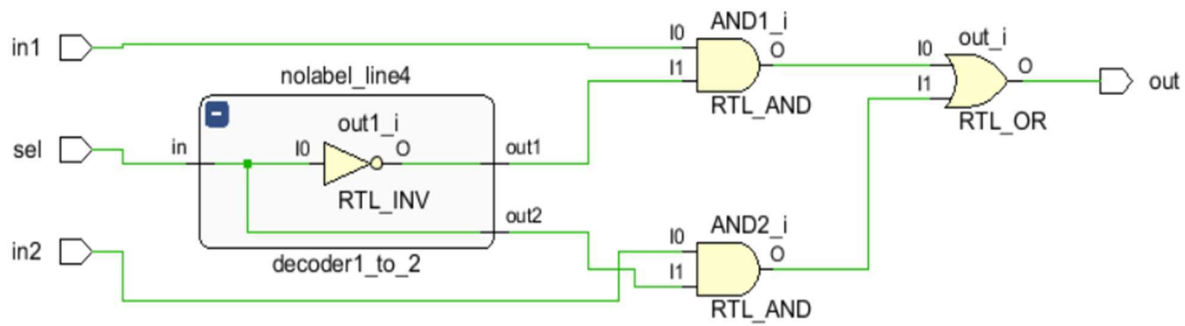


## 2) Exercise 2

a) Test bench for the 2-to-1 Multiplexer

- RTL code: This code represents the actual hardware design or behavior of the digital system. It describes how various registers and combinational logic elements are interconnected to perform a specific function.

- Testbench code: The testbench is used to verify the functionality of the RTL code. It generates input stimuli, applies them to the design under test, and checks the output responses against expected results.


Waveform:

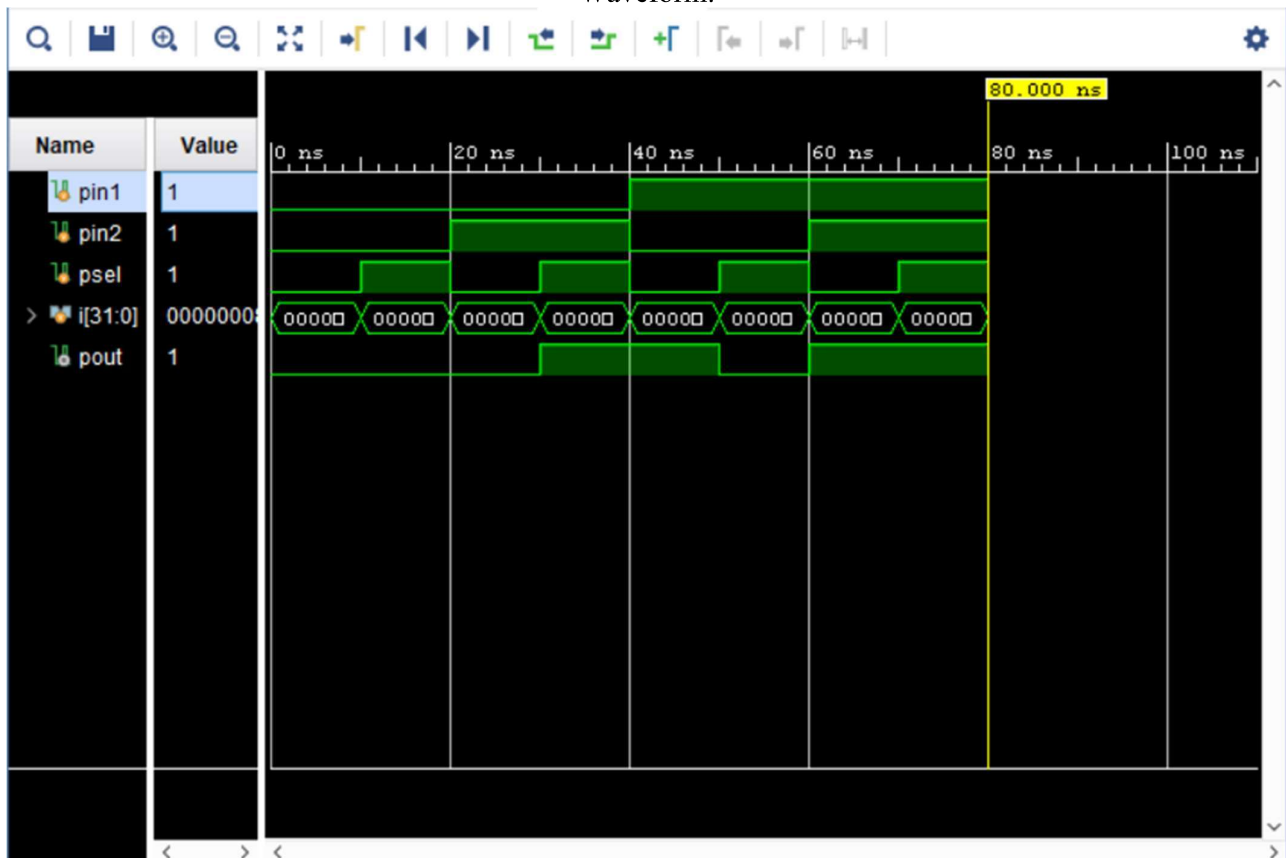



```
# run 1000ns
pin1=0, pin2=0, psel=0, pout=0
pin1=0, pin2=0, psel=1, pout=0
pin1=0, pin2=1, psel=0, pout=0
pin1=0, pin2=1, psel=1, pout=1
pin1=1, pin2=0, psel=0, pout=1
pin1=1, pin2=0, psel=1, pout=0
pin1=1, pin2=1, psel=0, pout=1
pin1=1, pin2=1, psel=1, pout=1
$finish called at time : 80 ns
```

 b) Compare the Synthesis's Schematic and the RTL Analysis's schematic



- Synthesis's Schematic represents the synthesized netlist derived from the RTL code.
- RTL Analysis's schematic represents the code by logic gates illustrating the data flow, and structure of the RTL code.

c) After that, run the Implementation, check the Utilization report in the Summary report in Project Summary for used resources.

Name	1	Slice LUTs (53200)	Slice (1330 0)	LUT as Logic (53200)	Bonded IOB (125)
N mul_2_to_1		1	1	1	4

3) Exercise 3:

a) Design a half-adder circuit using structural model.


 


Figure 3: Half-adder

 

c) Design a full-adder circuit using structural model. Reuse the half-adder module.



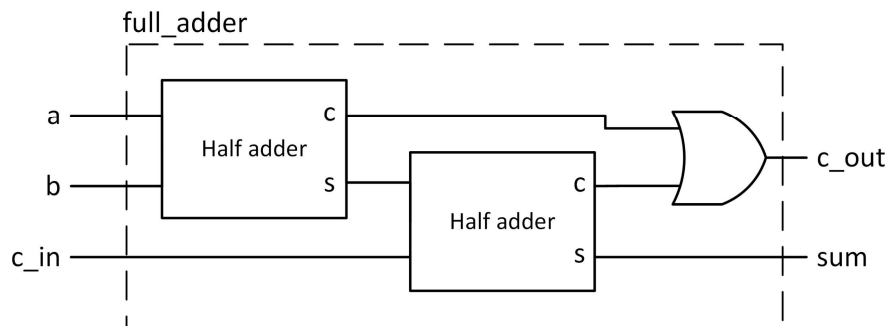


Figure 4: Full-adder

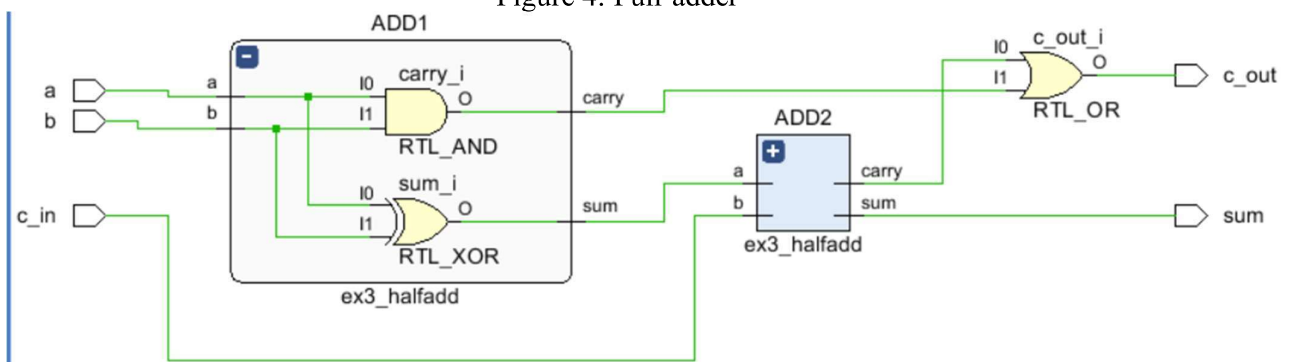

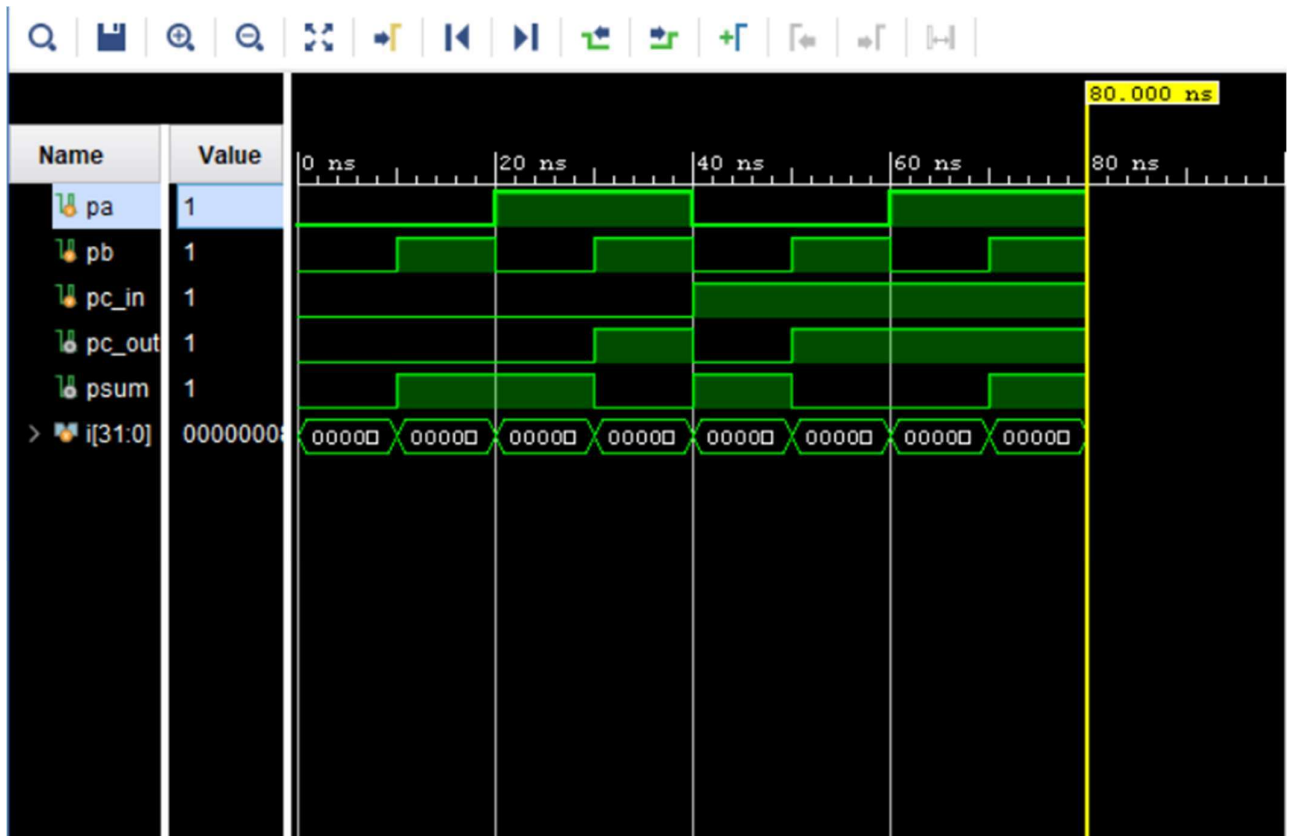Testbench to evaluate operations of the implemented full-adder circuit



d) Design a 4-bit ripple carry adder using structural model. Reuse the implemented full-adder.


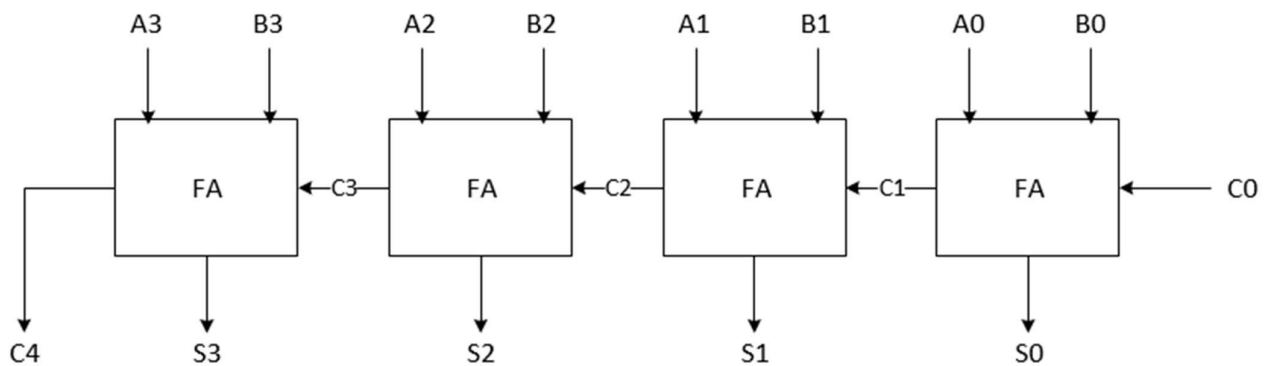


Figure 5: 4-bit ripple carry adder

 Testbench to simulate the implemented circuit:



#### 4) Exercise 4


 
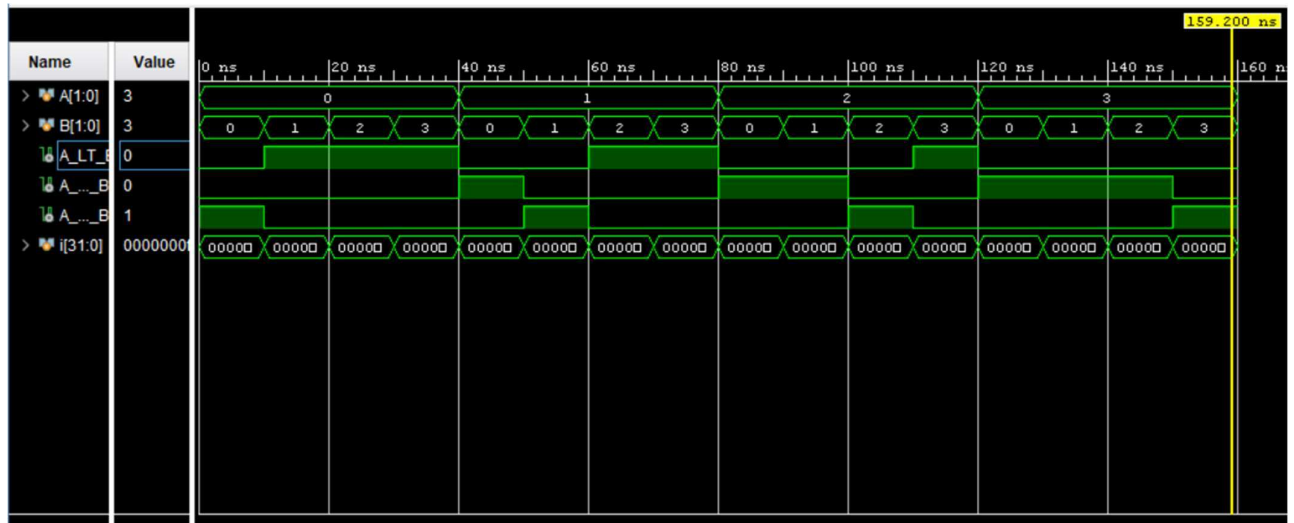


Figure 6: 2-bit comparator

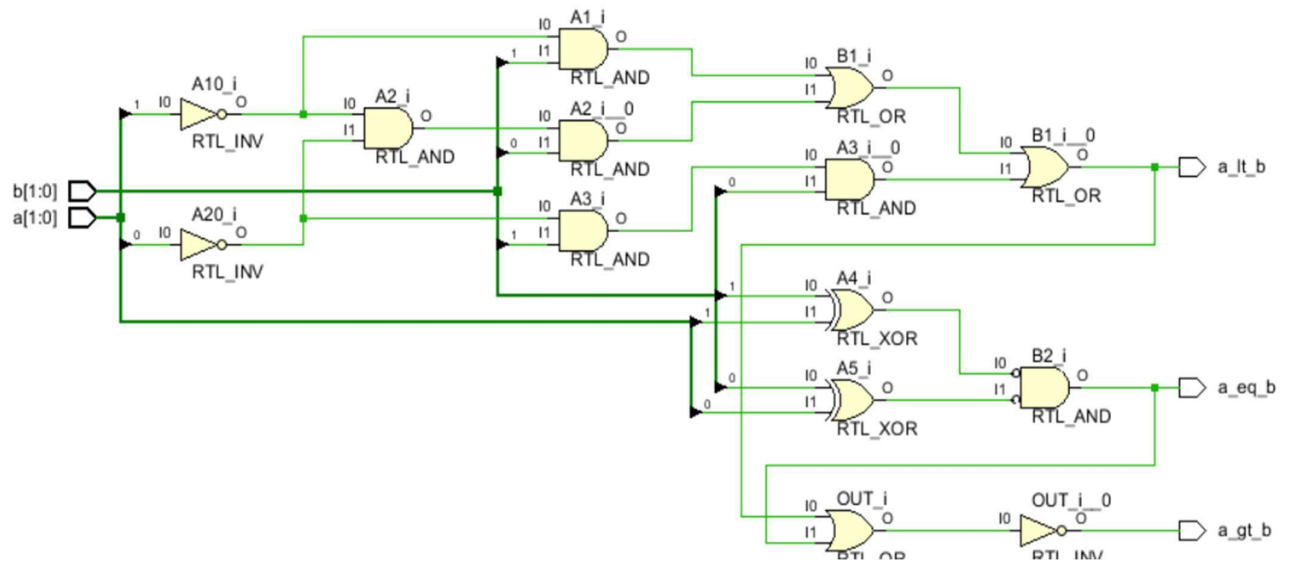

- The functions of each output of the 2-bit comparator:


$$a\_gt\_b = (\bar{a}_1b_1 + \bar{a}_1\bar{a}_0b_0 + \bar{a}_0b_1b_0)'((b_1a_1)(b_0a_0))' + (\bar{a}_1b_1 + \bar{a}_1\bar{a}_0b_0 + \bar{a}_0b_1b_0)(b_1a_1)(b_0a_0)$$

$$a\_lt\_b = \bar{a}_1b_1 + \bar{a}_1\bar{a}_0b_0 + \bar{a}_0b_1b_0$$

$$a\_eq\_b = (b_1a_1)(b_0a_0)$$

- Schematic of 4-bit comparator:



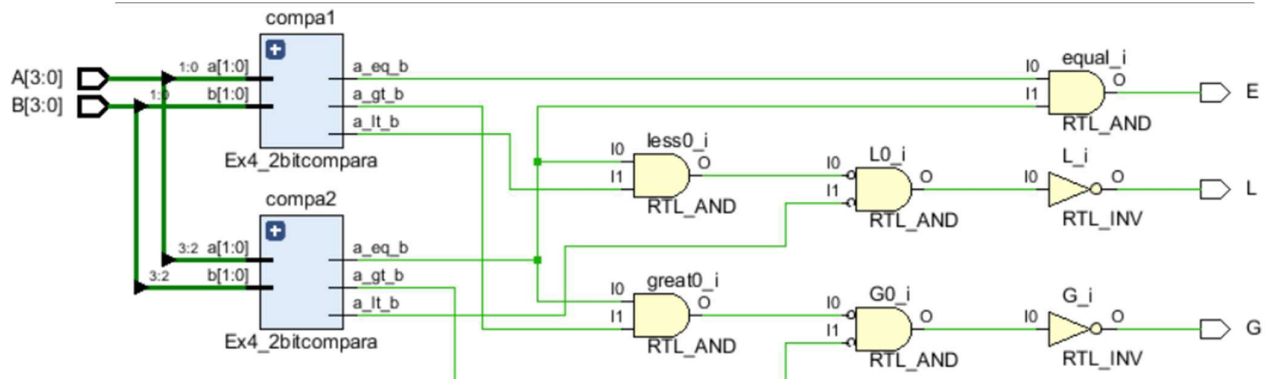

-Testbench waveform:

