

NATIONAL UNIVERSITY HO CHI MINH CITY
**UNIVERSITY OF TECHNOLOGY – FACULTY OF COMPUTER
SCIENCE AND ENGINEERING**



REPORT LAB 2
LOGIC DESIGN WITH HDL
ADVISOR: NGUYỄN THẾ BÌNH
TEAM 8

Name:	Students's ID
Phạm Anh Tài	2350023
Phạm Ngọc Huy	2352404
Trần Đình Duy Khương	2352638
Lục Tấn Phúc	2352935

I. Exercise:

2.1 Exercise 1 Design a circuit that has one 4-bit input and 4-bit output with functions as follow (all outputs are active HIGH):

- Output 0: active when there are even number of bit 1 in the input.
- Output 1: active when there are only 1 bit 1 in the input.
- Output 2: active when there is no bit 1 in the input.
- Output 3: active when all bit in the input are 1. Write Verilog HDL RTL code and test bench for the design. Test the circuit on FPGA using buttons and LEDs. Hint: Students should use reduction operators.

-Module code:

```
module lab2_ex1(input [3:0] in, output[3:0] out );

    assign out[0] = ^in;
    assign out[1] = ((in[3:0] & (in[3:0] - 1)) == 0) && (in[3:0] != 0);
    assign out[2] = ~|in;
    assign out[3] = &in;

endmodule
```


-Testbench code:

```
module tb_lab2_ex1;
    reg [3:0] pin;
    wire [3:0] pout;
    integer i;
    lab2_ex1 test(.in(pin), .out(pout));


    initial
    begin
        for(i=0;i<15;i=i+1)
        begin
            pin=i;
            #10;
        end
        $finish;
    end

endmodule
```

-RTL analysis:

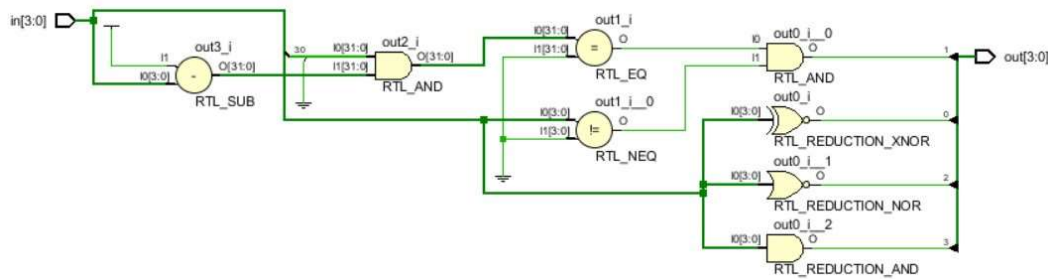

-Simulation:

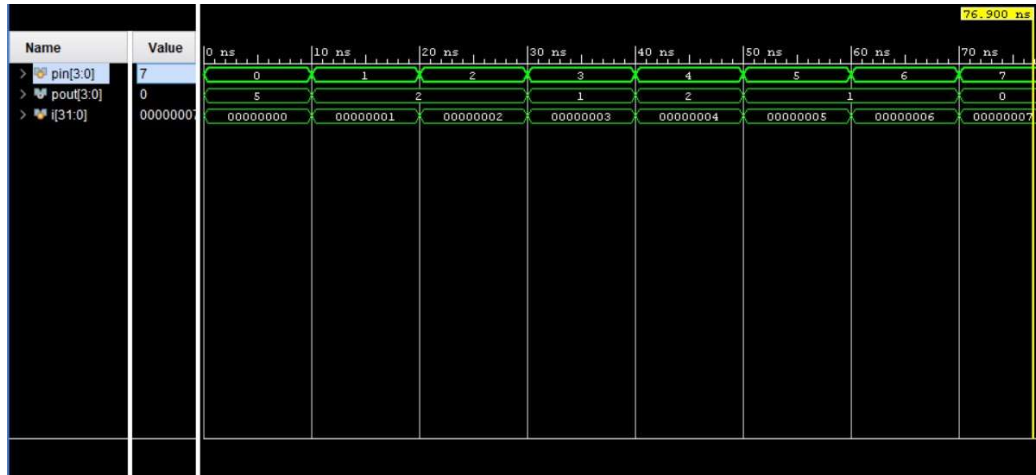

2.2 Exercise 2 Design a circuit that generate a 1 Hz output signal using behavioral model. This signal connect to LED on Arty-Z7 FPGA Board to make it blink (turn on for 0.5s - turn off for 0.5s). Know that the input clock frequency is 125 MHz. Write test benches to simulate the circuits. Test the circuits on FPGA board using LEDs or RGB LED.

-Module code:

```
module lab2_ex2(
    input clk125mhz,
    output clk1hz);

    reg [25:0] counter=0;

    always @(posedge clk125mhz )
        if(counter == 1_250_000 -1)
            counter <= 0;
        else counter <= counter +1;

    assign clk1hz = counter >=625_000;

endmodule
```

-Testbench code:

```

module tb_lab2_ex2;

reg clk125mhz;
wire clk1hz;


lab2_ex2 dut ( .clk125mhz(clk125mhz), .clk1hz(clk1hz));

initial
begin
clk125mhz=0;
    forever #400 clk125mhz=~clk125mhz;
end

endmodule

```

-Simulation:

 

2.3 Exercise 3 Design a 7-segment LED decoder which will accept a 4-bit input and generate a 7-bit output. • Interface: module bin2led7(enable, bin in, led out); • The enable signal controls LEDs. If enable = 0, LEDs are turned off. • The bin in is a 4-bit binary input signal. • The led out is a 7-bit output signal for 7-segment LED display.

-Module code:

```

22 |
23 | module lab2_ex3 (en, bin_in, led_out);
24 |
25 |     input [3:0] bin_in;
26 |     input en;
27 |     output reg [6:0] led_out;
28 |     always @*
29 |     begin
30 |         if(en==1'b0) led_out <= 7'd0;
31 |         else
32 |             case(bin_in)
33 |                 4'd0: led_out <= 7'd0;
34 |                 4'd1: led_out <= 7'b0110000;
35 |                 4'd2: led_out <= 7'b1101101;
36 |                 4'd3: led_out <= 7'b1111001;
37 |                 4'd4: led_out <= 7'b0110011;
38 |                 4'd5: led_out <= 7'b1011011;
39 |                 4'd6: led_out <= 7'b1011111;
40 |                 4'd7: led_out <= 7'b1110000;
41 |                 4'd8: led_out <= 7'b1111111;
42 |                 4'd9: led_out <= 7'b1111011;
43 |             endcase
44 |         end
45 |
46 |     endmodule
47 |

```


-Testbench code:

```


22 |
23 | module tb_lab2_ex3;
24 |     reg [3:0] bin_in;
25 |     wire [6:0] led_out;
26 |     reg en;
27 |
28 |     lab2_ex3 uut (.bin_in(bin_in), .en(en), .led_out(led_out));
29 |
30 | initial begin
31 |     en = 1'b0;
32 |     #10 en = 1'b1;
33 |     #10 bin_in <= 4'd1;
34 |     #10 bin_in <= 4'd2;
35 |     #10 bin_in <= 4'd3;
36 |     #10 bin_in <= 4'd4;
37 |     #10 bin_in <= 4'd5;
38 |     #10 bin_in <= 4'd6;
39 |     #10 bin_in <= 4'd7;
40 |     #10 bin_in <= 4'd8;
41 |     #10 bin_in <= 4'd9;
42 |
43 |     #10 en = 4'd0;
44 |     #10 bin_in <= 4'd1;
45 |     #20;
46 |     $finish;
47 | end
48 | endmodule
49 |

```

-RTL analysis:

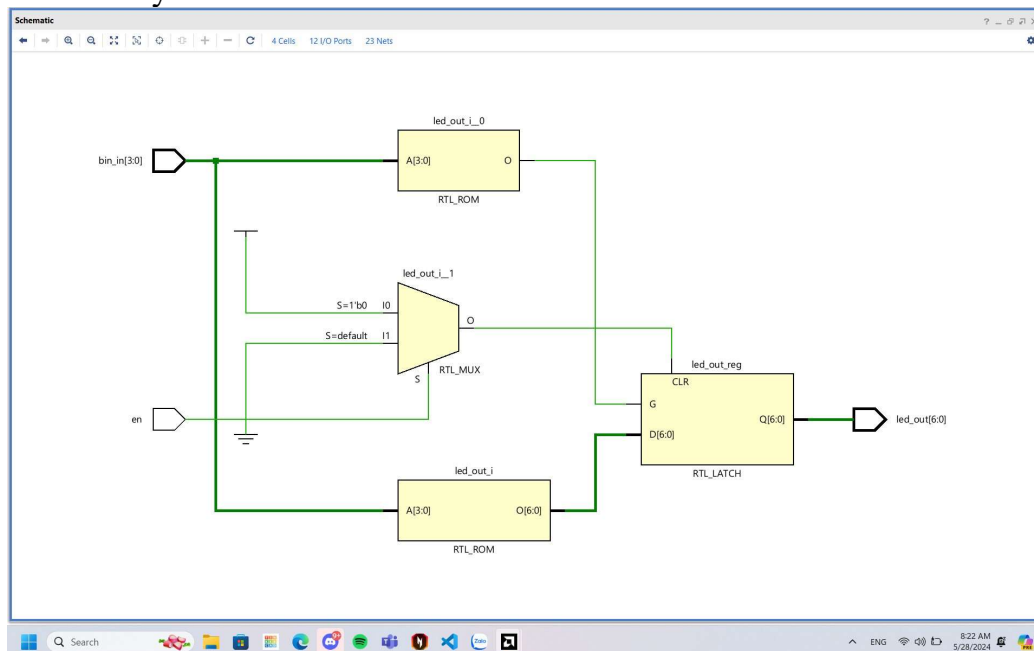

-Simulation:

 

2.4 Exercise 4 Design a circuit to control the RGB LEDs on Arty-Z7

board as follow: • Switch 0: select display mode - 1 LED or 2 LEDs. •

Switch 1:

– to select left or right LED in 1-LED display mode.

– to select color code as table below.

Write Verilog HDL RTL code and test bench for the design. Test the circuit on FPGA using switches, buttons and RGB LEDs on the Arty-Z7 board.

-Module code:

```

1 | `timescale 1ns / 1ps
2 | module rgb_led(bcd,mode,select,led);
3 |     input [3:0] bcd;
4 |     input mode; // sw0
5 |     input select; // sw1
6 |     output reg [5:0] led;
7 |
8 |     always @(bcd)
9 |     begin
10 |         if(mode == 1'b0)
11 |         begin
12 |             if(select == 1'b0)
13 |             begin
14 |                 case (bcd) //case statement
15 |                     0 : led = 6'b000000;
16 |                     1 : led = 6'b000001;
17 |                     2 : led = 6'b000010;
18 |                     4 : led = 6'b000100;
19 |                     8 : led = 6'b000111;
20 |                     default : led = 6'b000000;
21 |                 endcase
22 |             end
23 |             else
24 |             begin
25 |                 case (bcd) //case statement
26 |                     0 : led = 6'b000000;
27 |                     1 : led = 6'b001000;
28 |                     2 : led = 6'b010000;
29 |                     4 : led = 6'b100000;
30 |                     8 : led = 6'b110000;
31 |                     default : led = 6'b000000;
32 |                 endcase
33 |             end
34 |         end
35 |         else
36 |         begin
37 |             if(select == 1'b0)
38 |             begin
39 |                 case (bcd) //case statement
40 |                     0 : led = 6'b000000;
41 |                     1 : led = 6'b001001;
42 |                     2 : led = 6'b010010;
43 |                     4 : led = 6'b100100;
44 |                     8 : led = 6'b111111;
45 |                     default : led = 6'b000000;
46 |                 endcase
47 |             end
48 |             else
49 |             begin
50 |                 case (bcd) //case statement
51 |                     0 : led = 6'b000000;
52 |                     1 : led = 6'b011011;
53 |                     2 : led = 6'b110110;
54 |                     4 : led = 6'b101101;
55 |                     8 : led = 6'b111111;
56 |                     default : led = 6'b011011;
57 |                 endcase
58 |             end
59 |         end
60 |     end
61 | endmodule

```


-Testbench code:


```

module rgb_led_tb;
    reg [3:0] bcd;
    reg mode,select;
    wire [5:0] led;

    rgb_led UUT(bcd,mode,select,led);
    initial $monitor("%time: led=%b",$time,led);
    initial begin
        bcd=4'b0100; mode=1'b0; select=1'b0;
        #10
        bcd=4'b0100; mode=1'b1; select=1'b1;
        #10
        bcd=4'b0001; mode=1'b1; select=1'b0;
        #10
        bcd=4'b1101; mode=1'b0; select=1'b0;
    end
endmodule

```

- RTL analysis:

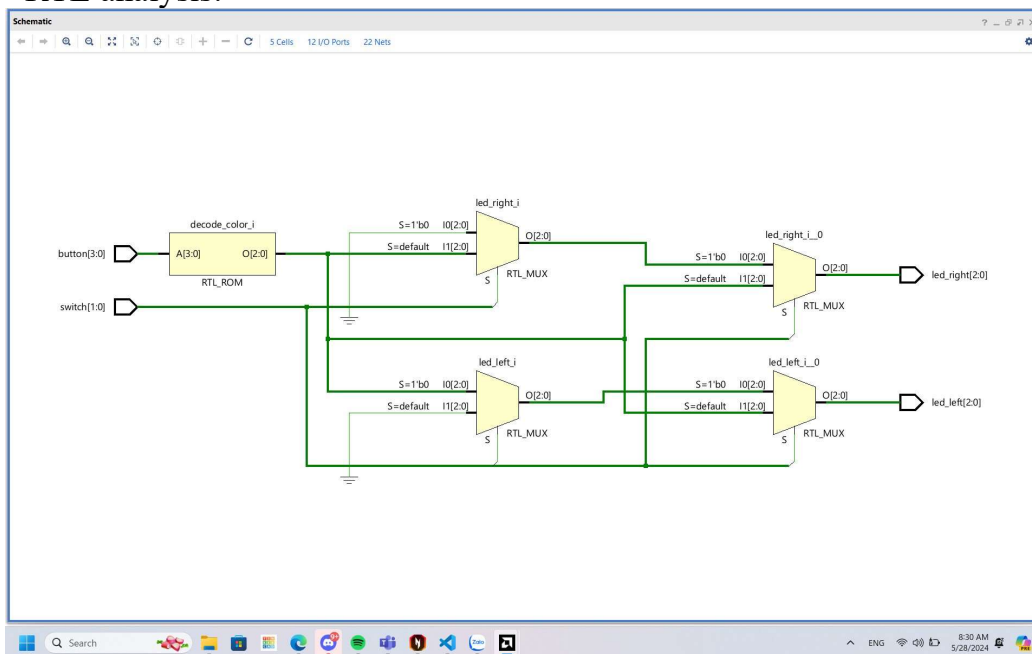

-Simulation:

